

# Contents

**R** Read for background    **O** Optional material

## Chapter 1 DC Circuits

<b>1.1</b>	<b>Introduction</b> .....	<b>1</b>
<b>1.2</b>	<b>Basic Concepts</b> .....	<b>1</b>
	1.2.1 Current, 2    1.2.2 Potentials, 2    1.2.3 The Electromotive Force or EMF, 3    1.2.4 Ohm's Law and Resistance, 3	
<b>1.3</b>	<b>The Schematic Diagram</b> .....	<b>4</b>
<b>1.4</b>	<b>Power in DC Circuits</b> .....	<b>6</b>
<b>1.5</b>	<b>Series and Parallel Connections</b> .....	<b>7</b>
	1.5.1 The Voltage Divider, 8    1.5.2 The Current Divider, 10	
<b>1.6</b>	<b>Kirchhoff's Laws</b> .....	<b>10</b>
	1.6.1 Branch Current Method, 11    1.6.2 Loop Current Method, 13	
<b>1.7</b>	<b>The Equivalent Circuit</b> .....	<b>15</b>
	1.7.1 Thevenin's and Norton's Theorems, 17    1.7.2 Determination of Thevenin and Norton Circuit Elements, 18    1.7.3 <sup>R</sup> Circuit Simplification with a Thevenin Equivalent, 18    1.7.4 <sup>O</sup> Reduction of a Two-Terminal Network, 21	
<b>1.8</b>	<b>Measurement</b> .....	<b>22</b>
	<b>Problems</b> .....	<b>27</b>

## Chapter 2 AC Circuits

<b>2.1</b>	<b>Introduction</b> .....	<b>33</b>
<b>2.2</b>	<b>AC Circuit Elements</b> .....	<b>33</b>
	2.2.1 Capacitance, 34    2.2.2 Inductance, 37	
<b>2.3</b>	<b>The Circuit Equations</b> .....	<b>39</b>
	2.3.1 The RC Circuit, 40    2.3.2 The LC Circuit, 41 2.3.3 The LCR Circuit, 43	
<b>2.4</b>	<b>AC Signals</b> .....	<b>44</b>
<b>2.5</b>	<b>Phasors</b> .....	<b>47</b>
<b>2.6</b>	<b>AC Signal Sources</b> .....	<b>49</b>

<b>2.7</b>	<b>Circuits with Sinusoidal Sources and the Complex Impedance . . . . .</b>	<b>52</b>
	2.7.1 Resistive Impedance, 52 2.7.2 Inductive Impedance, 53	
	2.7.3 Capacitive Impedance, 54 2.7.4 Combined Impedances, 55	
	2.7.5 Phase Angle Between Voltage and Current, 58	
<b>2.8</b>	<b>Resonance . . . . .</b>	<b>61</b>
	2.8.1 Q Factor, 63	
<b>2.9</b>	<b>Four-Terminal Networks . . . . .</b>	<b>67</b>
<b>2.10</b>	<b>Bode Plots . . . . .</b>	<b>68</b>
	2.10.1 Single-Term Approximations of $H(j\omega)$ , 68	
<b>2.11<sup>R</sup></b>	<b>AC Equivalent Circuits . . . . .</b>	<b>71</b>
	2.11.1 <sup>R</sup> The Four Terminal AC Equivalent Circuit, 71	
	2.11.2 <sup>R</sup> Input and Output Impedances of the Four-Terminal Network, 73	
	2.11.3 <sup>R</sup> Four-Terminal Equivalent Circuit for a Buffered Amplifier, 76	
	2.12 Power in AC Circuits, 77	
	<b>Problems . . . . .</b>	<b>79</b>

### *Chapter 3 Signals, Filters, and Amplifiers*

<b>3.1</b>	<b>Introduction . . . . .</b>	<b>84</b>
<b>3.2</b>	<b>The Principle of Superposition and Signal Analysis . . . . .</b>	<b>84</b>
	3.2-1 Fourier Series, 85	
<b>3.3</b>	<b>Filters and Amplifiers . . . . .</b>	<b>88</b>
<b>3.4</b>	<b>Types of Filters . . . . .</b>	<b>89</b>
<b>3.5</b>	<b>Bode Plots and Decibels . . . . .</b>	<b>90</b>
<b>3.6</b>	<b>Passive RC Filters . . . . .</b>	<b>92</b>
	3.6.1 Low-Pass Filter, 92 3.6.2 <sup>R</sup> Approximate Integrator, 97	
	3.6.3 High-Pass Filter, 99 3.6.4 Approximate Differentiator, 101	
<b>3.7</b>	<b>Complex Frequencies and the s-Plane . . . . .</b>	<b>102</b>
	3.7.1 The Poles and Zeros of $H$ , 102 3.7.2 Frequency Response from Poles and Zeros, 104	
<b>3.8</b>	<b>The Impulse Response of a Four-Terminal Network . . . . .</b>	<b>106</b>

<b>3.9<sup>R</sup></b>	<b>Sequential RC Filters</b> .....	<b>108</b>
<b>3.10</b>	<b>Passive LCR Filters</b> .....	<b>112</b>
	3.10.1 The Series LCR Circuit, 112 3.10.2 The Tank Circuit, 117	
<b>3.11<sup>R</sup></b>	<b>RC Band-rejection Filters</b> .....	<b>117</b>
	3.11.1 <sup>R</sup> Bridged T, 118 3.11.2 Twin T, 119	
<b>3.12</b>	<b>Amplifier Model</b> .....	<b>120</b>
	3.12.1 One-, Two-, and Three-Pole Models, 121 3.12.2 Amplifier with Negative Feedback, 123	
	<b>Problems</b> .....	<b>125</b>

## *Chapter 4 Transformers*

<b>4.1<sup>O</sup></b>	<b>Introduction</b> .....	<b>130</b>
<b>4.2<sup>O</sup></b>	<b>Transformer Equations</b> .....	<b>132</b>
	4.2.1 <sup>O</sup> Time-Independent Equations, 135 4.2.2 <sup>O</sup> Voltage and Current Transfer Functions, 136 4.2.3 <sup>O</sup> The Input Impedance, 137 4.2.4 <sup>O</sup> Output Impedance, 142	
<b>4.3<sup>O</sup></b>	<b>A More Complete Transformer Model</b> .....	<b>144</b>
	<b>Problems</b> .....	<b>146</b>

## *Chapter 5 The PN Junction and Diode Circuits*

<b>5.1</b>	<b>Introduction</b> .....	<b>150</b>
<b>5.2<sup>R</sup></b>	<b>Atoms and Energy Levels</b> .....	<b>151</b>
<b>5.3<sup>R</sup></b>	<b>Energy Levels in Crystalline Solids</b> .....	<b>152</b>
<b>5.4</b>	<b>The PN Junction and the Diode Effect</b> .....	<b>156</b>
	5.4.1 Current in the Diode, 158 5.4.2 The PN Diode as a Circuit Element, 162 5.4.3 The Zener Diode, 165 5.4.4 <sup>O</sup> Light-Emitting Diodes, 169 5.4.5 <sup>O</sup> Light-Sensitive Diodes, 169	

<b>5.5</b>	<b>Circuit-Applications of Ordinary Diodes</b> .....	<b>171</b>
	5.5.1 Rectifiers, 172 5.5.2 Clamping, 173 5.5.3 Clipping, 176	
	5.5.4 <sup>0</sup> The Charge Pump, 176 5.5.5 <sup>R</sup> The Frequency-to-Voltage Converter, 178	
	5.5.6 <sup>0</sup> The Voltage Doubler, 179 5.5.7 Inductive Surge Suppression, 180	
<b>5.6</b>	<b>Power Supplies</b> .....	<b>181</b>
	5.6.1 Integrated Circuit Voltage Regulators, 184	
	<b>Problems</b> .....	<b>185</b>

## *Chapter 6 Single Transistor Circuits*

<b>6.1</b>	<b>Introduction</b> .....	<b>189</b>
<b>6.2<sup>R</sup></b>	<b>Bipolar Transistors</b> .....	<b>190</b>
	6.2.1 <sup>R</sup> The NPN Transistor: Principles of Operation, 191 6.2.2 Basic Circuit Configurations, 195	
	6.2.3 Small-Signal Models, 197 6.2.4 Ideal and Perfect Bipolar Transistor Models, 201	
	6.2.5 Ideal Transistor Working Rules, 202 6.2.6 <sup>0</sup> Transconductance Model, 203	
<b>6.3</b>	<b>The Common Emitter Amplifier</b> .....	<b>203</b>
	6.3.1 DC Biasing, 204 6.3.2 Equivalent Circuit for AC Signals, 210	
	6.3.3 Approximate AC Model, 210 6.3.4 The Basic CE Amplifier, 211	
	6.3.5 <sup>0</sup> High-Frequency Operation, 213	
	6.3.6 CE Amplifier with Emitter Resistor, 215	
<b>6.4</b>	<b>The Common Collector Amplifier</b> .....	<b>218</b>
	6.4.1 Voltage Gain, 218 6.4.2 Input and Output Impedances, 218	
<b>6.5<sup>0</sup></b>	<b>The Common Base Amplifier</b> .....	<b>222</b>
	6.5.1 <sup>0</sup> DC Biasing, 222 6.5.2 <sup>0</sup> Voltage Gain, 222	
	6.5.3 <sup>0</sup> Input and Output Impedances, 223	
<b>6.6</b>	<b>The PNP Transistor</b> .....	<b>224</b>
<b>6.7</b>	<b>Current Sources</b> .....	<b>225</b>
<b>6.8</b>	<b>The Junction Field Effect Transistor (JFET)</b> .....	<b>226</b>
	6.8.1 Principles of Operation, 226 6.8.2 Variable-Resistance Operation, 229	
	6.8.3 DC Biasing, 229 6.8.4 Small-Signal AC Model, 231	
<b>6.9</b>	<b>JFET Common Source Amplifier</b> .....	<b>232</b>
	6.9.1 Low-Frequency Analysis, 233 6.9.2 High-Frequency Operation, 235	
	6.9.3 <sup>0</sup> Reactive Loads and Resonant Circuits, 238	

<b>6.10<sup>0</sup> JFET Common Drain Amplifier</b> .....	<b>240</b>
6.10.1 <sup>0</sup> Voltage Gain, 240	
6.10.2 <sup>0</sup> Input and Output Impedances, 240	
<b>6.11<sup>0</sup> The Insulated-Gate Field Effect Transistor (IGFET)</b> .....	<b>241</b>
6.11.1 <sup>0</sup> Enhancement and/or Depletion: Principles of Operation, 242	
6.11.2 <sup>0</sup> DC Biasing and AC Analysis, 244	
<b>6.12<sup>0</sup> Power MOSFET Circuits</b> .....	<b>245</b>
<b>6.13<sup>0</sup> Switching an Inductive Load</b> .....	<b>246</b>
<b>Problems</b> .....	<b>247</b>

## *Chapter 7 Multiple Transistor Circuits*

<b>7.1 Introduction</b> .....	<b>255</b>
<b>7.2<sup>0</sup> Coupling Between Single Transistor Stages</b> .....	<b>255</b>
7.2.1 <sup>0</sup> Capacitive Coupling, 256	
7.2.2 <sup>0</sup> Transformer Coupling, 259	
<b>7.3 Darlington and Sziklai Connections</b> .....	<b>262</b>
<b>7.4<sup>0</sup> Current Source as an Emitter Load</b> .....	<b>264</b>
<b>7.5 Cascode Connection</b> .....	<b>265</b>
<b>7.6<sup>0</sup> MOSFET Biasing with a Current Source</b> .....	<b>267</b>
<b>7.7 Matched Transistor Pairs</b> .....	<b>268</b>
<b>7.8 Current Mirror</b> .....	<b>268</b>
<b>7.9 Differential Amplifier</b> .....	<b>269</b>
7.9.1 <sup>0</sup> Differential Amplifiers with Active Loads, 273	
<b>7.10 Push-Pull output Stages</b> .....	<b>275</b>
7.10.1 Push-Pull with Bipolar Transistors, 278	
7.10.2 <sup>0</sup> Totem Pole Output Stage, 281	
<b>7.11<sup>R</sup> Reading an Integrated Circuit Schematic</b> .....	<b>281</b>
<b>Problems</b> .....	<b>283</b>

## *Chapter 8 Operational Amplifiers*

<b>8.1</b>	<b>Introduction</b> .....	<b>288</b>
<b>8.2</b>	<b>Open-Loop Amplifier</b> .....	<b>289</b>
<b>8.3</b>	<b>Ideal Amplifier Approximation</b> .....	<b>291</b>
	8.3.1 Noninverting Amplifiers, 292    8.3.2 Inverting Amplifiers, 293	
	8.3.3 Current Summing Junction, 294    8.3.4 Differentiation Circuit, 296	
	8.3.5 Integration circuit, 298    8.3.6 Active Filters, 300	
	8.3.7 <sup>o</sup> General Feedback Elements, 303    8.3.8 Differential Amplifiers, 305	
	8.3.9 <sup>o</sup> Perfect Diodes, 307    8.3.10 <sup>o</sup> The Negative Impedance Converter (NIC), 308	
	8.3.11 <sup>o</sup> The Gyrator, 310    8.3.12 <sup>R</sup> The Wein Bridge Oscillator, 311	
	8.3.13 Voltage-to-Current Converters, 313	
	8.3.14 <sup>R</sup> Power Drivers, 314	
<b>8.4</b>	<b>Analysis Using Finite Open-loop Gain</b> .....	<b>316</b>
	8.4.1 Output Impedance, 317    8.4.2 Current Limiting and Slew Rate, 319	
	8.4.3 Input Impedance, 321    8.4.4 The Notch Filter, 322    8.4.5 <sup>o</sup> Voltage and Current Offsets, 326	
<b>8.5</b>	<b>Feedback-induced Oscillations</b> .....	<b>328</b>
<b>8.6</b>	<b>Pole-Zero Analysis</b> .....	<b>329</b>
	8.6.1 Zero-Slope Closed-Loop Gain, 330	
	8.6.2 Positive-Slope Closed-Loop Gain, 332	
<b>8.7<sup>o</sup></b>	<b>Nyquist Plot</b> .....	<b>335</b>
	<b>Problems</b> .....	<b>338</b>

## *Chapter 9 Digital Circuits*

<b>9.1</b>	<b>Introduction</b> .....	<b>346</b>
<b>9.2</b>	<b>The Transistor as a Switch</b> .....	<b>346</b>
<b>9.3</b>	<b>Number Systems</b> .....	<b>348</b>
	9.3.1 Binary Numbers, 348    9.3.2 Octal and Hexadecimal Numbers, 350	
	9.3.3 Nibbles, Bytes, and Words, 351	
<b>9.4</b>	<b>Boolean Algebra</b> .....	<b>353</b>
	9.4.1 Theorems, 354	
<b>9.5</b>	<b>Logic Gates</b> .....	<b>354</b>
	9.5.1 The Basic Gates, 355    9.5.2 Implementation with Diodes, 355	

<b>9.6</b>	<b>Combinational Logic</b> .....	<b>358</b>
	9.6.1 The AND-OR Gate, 358 9.6.2 Combinational Logic Design Using Truth Tables, 359 9.6.3 Exclusive-OR Gate, 361 9.6.4 Timing Diagrams, 361 9.6.5 Signal Race, 365 9.6.6 Half and Full Adders, 365 9.6.7 <sup>0</sup> Minterms and Karnaugh Maps, 368	
<b>9.7</b>	<b>Multiplexers and Decoders</b> .....	<b>374</b>
<b>9.8</b>	<b>Schmitt Trigger</b> .....	<b>376</b>
<b>9.9<sup>R</sup></b>	<b>Logic Families</b> .....	<b>377</b>
	9.9.1 <sup>R</sup> Transistor-Transistor (TTL), 377 9.9.2 <sup>R</sup> Complementary Metal Oxide Semiconductor (CMOS), 379 9.9.3 <sup>R</sup> Emitter-Coupled Logic (ECL), 380	
<b>9.10</b>	<b>The Data Bus</b> .....	<b>381</b>
	9.10.1 Wired ANDs and Ors, 381 9.10.2 Three-State Outputs, 382	
<b>9.11</b>	<b>Two-State Storage Elements</b> .....	<b>383</b>
<b>9.12</b>	<b>Latches and Unclocked Flip-flops</b> .....	<b>384</b>
	9.12.1 Latches, 384 9.12.2 RS and $\overline{R} \overline{S}$ Flip-flops, 385	
<b>9.13</b>	<b>Clocked Flip-flops</b> .....	<b>387</b>
	9.13.1 Clocked AS Flip flop, 387 9.13.2 DFlip-flop, 386 9.13.3 JK Flip-flop, 389	
<b>9.14</b>	<b>Dynamically Clocked Flip-flops</b> .....	<b>390</b>
	9.14.1 Master/Slave or Pulse Triggering, 391 9.14.2 Edge Triggering, 392	
<b>9.15</b>	<b>One-shots</b> .....	<b>395</b>
<b>9.16<sup>R</sup></b>	<b>State Diagrams</b> .....	<b>396</b>
<b>9.17</b>	<b>Registers</b> .....	<b>398</b>
	9.17.1 Data Registers, 398 9.17.2 Shift Registers, 400 9.17.3 Counters, 400 9.17.4 <sup>0</sup> Divide-by-N Counters, 403	
	<b>Problems</b> .....	<b>404</b>

## *Chapter 10 Data Acquisition and Process Control*

<b>10.1</b>	<b>Introduction</b> .....	<b>408</b>
<b>10.2</b>	<b>Typical Computer Application</b> .....	<b>408</b>
<b>10.3</b>	<b>Signal Domains</b> .....	<b>410</b>

<b>10.4</b>	<b>Input Transducers</b> .....	<b>410</b>
<b>10.5</b>	<b>Output Transducers</b> .....	<b>414</b>
<b>10.6</b>	<b>Signal Conditioning Circuits</b> .....	<b>415</b>
	10.6.1 Debouncing the Mechanical Switch, 419	
	10.6.2 Op Amps for Gain, Offset, and Function Modification, 419	
	10.6.3 Bridge Circuits, 422 10.6.4 Analog Switches, 424	
	10.6.5 Sample-and-Hold Amplifiers, 425 10.6.6 Gated Charge-to-Voltage Amp[ifier, 429 10.6.7 Comparators, 430	
<b>10.7</b>	<b>Oscillators</b> .....	<b>432</b>
	10.7.1 Relaxation Oscillator, 432 10.7.2 TTL Digital Oscillators, 434	
	10.7.3 The 555 Timer, 435 10.7.4 Application to Interval Timers, 438	
<b>10.8</b>	<b>Digital-to-Analog Conversion</b> .....	<b>439</b>
	10.8.1 Current Summing and IC Devices, 439	
	10.8.2 DAC Limitations, 442 10.8.3 DAC Applications, 442	
<b>10.9</b>	<b>Analog-to-Digital Conversion</b> .....	<b>446</b>
	10.9.1 Parallel-Encoding ADC, 447 10.9.2 Successive Approximation ADC, 448 10.9.3 Dual-Slope ADC, 448	
<b>10.10</b>	<b>Time-to-Digital Conversion</b> .....	<b>451</b>
<b>10.11</b>	<b>Voltage-to-Frequency Conversion</b> .....	<b>452</b>
<b>10.12</b>	<b>Phase-Locked Loop</b> .....	<b>456</b>
	<b>Problems</b> .....	<b>458</b>

## *Chapter 11 Computers and Device Interconnection*

<b>11.1</b>	<b>Introduction</b> .....	<b>461</b>
<b>11.2</b>	<b>Elements of the Microcomputer</b> .....	<b>462</b>
	11.2.1 Microprocessors and Microcomputers, 462	
	11.2.2 Functional Elements of the Computer, 463	
	11.2.3 Mechanical Arrangement, 464 11.2.4 Addressing Devices on the Bus, 466 11.2.5 Control of the Bus, 469 11.2.6 Clock Lines and Timing Diagrams, 469 11.2.7 RAM Memory, Static and Dynamic, 470	
	11.2.8 ROM Memory, 472 11.2.9 I/O Ports, 473	
	11.2.10 Interrupts, 473	
<b>11.3</b>	<b>The 8-, 16-, or 32-Bit Choice</b> .....	<b>475</b>
	11.3.1 Intel 8080, Zilog Z80, 476 11.3.2 Intel 8088, 476	
	11.3.3 Motorola 68000-66020, 478	

<b>11.4</b>	<b>Auxiliary LSI Devices</b> .....	<b>479</b>
<b>11.5</b>	<b>Standard Device Interfaces</b> .....	<b>481</b>
	11.5.1 Bit-Serial Asynchronous RS232C, 482	11.5.2 Modems, 485
	11.5.3 Byte-Serial: IEEE 488, 486	11.5.4 Word-Serial: CAMAC, 487
<b>11.6</b>	<b>Device Interconnection</b> .....	<b>488</b>
	11.6.1 Low Impedance Lines, 488	11.6.2 High-Impedance Lines, 492
	11.6.3 Grounds and Induced Signals, 496	11.6.4 Bypass Capacitors, 498
	<b>Problems</b> .....	<b>499</b>

## *Chapter 12 Signal Analysis*

<b>12.1</b>	<b>Introduction</b> .....	<b>502</b>
<b>12.2</b>	<b>Frequency-Domain Signal Analysis</b> .....	<b>503</b>
	12.2.1 Complex Fourier Series, 503	12.2.2 Fourier Transform, 503
	12.2.3 The Delta Function, 505	12.2.4 Fourier Transform Applications, 506
	12.2.5 The Laplace Transform, 513	
<b>12.3</b>	<b>Time-Domain Signal Analysis</b> .....	<b>514</b>
<b>12.4</b>	<b>Connection Between the Time and Frequency Domains</b> .....	<b>517</b>
	12.4.1 Poles and Zeros in $H(s)$ and the Impulse Response Function $h(t)$ , 518	12.4.2 Impulse Response and the Q of an LCR Circuit, 523
	12.4.3 Identifying the Most Persistent Term in $h(t)$ , 525	
<b>12.5</b>	<b>Intuitive Techniques</b> .....	<b>526</b>
	<b>Problems</b> .....	<b>527</b>

## *Chapter 13 Noise and Statistics*

<b>13.1</b>	<b>Introduction</b> .....	<b>530</b>
<b>13.2</b>	<b>Statistical Description of Signals with Random Noise Content</b> .....	<b>530</b>
	13.2.1 The Measurement Process, 531	13.2.2 The Ergodic Assumption and Time Averages, 534

<b>13.3</b>	<b>Probability Density Distributions</b> .....	<b>535</b>
	13.3.1 Poisson Distribution, 536 13.3.2 Gaussian Distribution, 539	
	13.3.3. Sum of Random Variables, 541	
<b>13.4</b>	<b>Random Noise in Electronic Systems</b> .....	<b>543</b>
	13.4.1 Thermal or Johnson Noise, 543 13.4.2 Counting Statistics or Shot	
	Noise, 545 13.4.3 Flicker or 1/f Noise, 548 13.4.4 Modeling the Noise in	
	Real Amplifiers, 549 13.4.5 Techniques Used to Extract Signal from Noise,	
	551	
<b>13.5</b>	<b>Multivariable Analysis</b> .....	<b>552</b>
	13.5.1 Autocorrelation and Cross-correlation Functions, 552	
	13.5.2 Comparison of Convolution and Correlation Integrals, 554	
<b>13.6</b>	<b>The Power Spectrum</b> .....	<b>556</b>
	13.6.1 Fourier Transform of the Correlation Integral, 556 13.6.2 Power	
	Signals in the Time and Frequency Domains, 557 13.6.3 The Causal	
	Signal, 559 13.6.4 Autocorrelation Function of Band-Limited White Noise,	
	561 13.6.5 Autocorrelation Applications, 562 13.6.6 Coherence Time	
	for Real Signal Generator, 563	
<b>13.7</b>	<b>Cross-correlation Applications</b> .....	<b>564</b>
<b>13.8</b>	<b>Signal Analyzer Block Diagrams</b> .....	<b>566</b>
	<b>Problems</b> .....	<b>567</b>

## *Chapter 14 Discrete Signal Analysis*

<b>14.1</b>	<b>Introduction</b> .....	<b>572</b>
<b>14.2</b>	<b>Sampled Signals</b> .....	<b>572</b>
	14.2.1 Complex Signal Representation, 574 14.2.2 The Nyquist	
	Frequency Limit, 574	
<b>14.3</b>	<b>Filtering Sampled Data</b> .....	<b>579</b>
	14.3.1 Moving-Average Filter Example, 582	
<b>14.4</b>	<b>Z-Transform</b> .....	<b>583</b>
<b>14.5</b>	<b>Digital Filters</b> .....	<b>586</b>
	14.5.1 The Recursive Filter, 586	
<b>14.6</b>	<b>Simulating an Analog Filter</b> .....	<b>590</b>
	14.6.1 Matching the impulse Response, 590 14.6.2 Mapping Poles and	
	Zeros, 592 14.6.3 Bilinear Transformation, 592	

<b>14.7 Discrete Fourier Transform</b> .....	<b>593</b>
14.7.1 Discrete Fourier Transform Theorems, 597	
14.7.2 The Ultimate Discrete Signal Filter, 599	
<b>14.8 Fast Fourier Transform</b> .....	<b>599</b>
14.8.1 The FFT Algorithm, 600	
14.8.2 FORTRAN Implementation for Microcomputers, 603	
<b>14.9 Cyclic Convolution and Correlation</b> .....	<b>605</b>
<b>14.10 Applications</b> .....	<b>607</b>
<b>Problems</b> .....	<b>607</b>

### *Appendixes*

- A. Solution of Three Equations in Three Unknowns by the Method of Determinants, 610
- B. The Miller Effect, 612
- C. Bipolar Transistor Amplifier with Collector-to-Base Feedback, 614

<b>Bibliography</b> .....	<b>617</b>
<b>Index</b> .....	<b>619</b>